

طراحی سیستم های دیجیتال
تمرین سوم
مهندسی کامپیوتر، دانشگاه شهید بهشتی

پدرام رمضان زاده
۹۹۲۴۳۰۸۵

عباس یزدان مهر
۹۹۲۴۳۰۷۷

۱۸ آذر ۱۴۰۱

	assignment	true or false
a	a <= x(2);	false
b	b <= x(2);	true
c	b <= y(3,5);	true
d	b <= w(5)(3);	false
e	y(1)(0) <= z(7);	false
f	x(0) <= y(0,0);	true
g	x <= "1110000";	true
h	a <= "0000000";	false
i	y(1) <= x;	false
j	w(0) <= y;	false
k	w(1) <= (7=>'1', OTHERS=>'0');	true
l	y(1) <= (0=>'0', OTHERS=>'1');	false
m	w(2)(7 DOWNT0 0) <= x;	true
n	w(0)(7 DOWNT0 6) <= z(5 DOWNT0 4);	false
o	x(3) <= x(5 DOWNT0 5);	true
p	b <= x(5 DOWNT0 5);	true
q	y <= ((OTHERS=>'0'), (OTHERS=>'0'), (OTHERS=>'0'), "10000001");	true
r	z(6) <= x(5);	true
s	z(6 DOWNT0 4) <= x(5 DOWNT0 3);	false
t	z(6 DOWNT0 4) <= y(5 DOWNT0 3);	false
u	y(6 DOWNT0 4) <= z(3 TO 5);	false
v	y(0, 7 DOWNT0 0) <= z;	true
w	w(2,2) <= '1';	false

ROM module code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity rom_8_x_4 is
    generic (
        address_width: integer := 8;
        address_bits: integer := 3;
        data_width: integer := 4
    );
    port (
        address: in std_logic_vector(address_bits-1 downto 0);
        data: out std_logic_vector(data_width-1 downto 0)
    );
end rom_8_x_4;

architecture Behavioral of rom_8_x_4 is
    type rom_type is array (0 to 8-1) of std_logic_vector(4-1 downto 0);
    signal my_rom : rom_type := (
        "0001",
        "0010",
        "0011",
        "0100",
        "0101",
        "0110",
        "0111",
        "1000"
    );
begin
    data <= my_rom (to_integer(unsigned(address)));
end Behavioral;

```

Testbench code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb is
end tb;

architecture Behavioral of tb is
    signal address: std_logic_vector(3-1 downto 0);
    signal data: std_logic_vector(4-1 downto 0);
begin
    my_rom8x4: entity work.rom_8_x_4 port map (address => address, data => data);
    address <= "000",
        "001" after 10 ns,
        "011" after 20 ns,
        "111" after 30 ns,


```

```

        "100" after 40 ns;
end Behavioral;

```

Output:

 


۳

	assignment	result
a	$x1 \leftarrow a \& c;$	$x1 \leftarrow "10010"$
b	$x2 \leftarrow c \& b;$	$x2 \leftarrow "00101100"$
c	$x3 \leftarrow b \text{ XOR } c;$	$x3 \leftarrow "1110"$
d	$x4 \leftarrow a \text{ NOR } b(3);$	$x4 \leftarrow '0'$
e	$x5 \leftarrow b \text{ sll } 2;$	$x5 \leftarrow "0000"$
f	$x6 \leftarrow b \text{ sla } 2;$	$x6 \leftarrow "0000"$
g	$x7 \leftarrow b \text{ rol } 2;$	$x7 \leftarrow "0011"$
h	$x8 \leftarrow a \text{ AND NOT } b(0) \text{ AND NOT } c(1);$	$x8 \leftarrow '0'$
i	$d \leftarrow (5 \Rightarrow '0', \text{OTHERS} \Rightarrow '1');$	$d \leftarrow "11011111"$

۴

 ابتدا باید ماشین حالات مورد نظر سوال را طراحی کنیم که به شکل زیر خواهد بود:



۴

System module code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_system is
    port (
        sensor: in std_logic;
        trafficlights: out std_logic_vector (4 downto 0)
    );
end my_system;

architecture Behavioral of my_system is
    type state_type is (s_g_r, s_y_r, s_r_g); -- s = state, green = g, red = r, yellow = y

    signal state: state_type;

begin

    sensor_event:
    process (sensor)
    begin
        -- rising edge
        if sensor'event and sensor = '1' then
            if state = s_g_r then
                state <= s_y_r, s_r_g after 5 ns;
            end if;
        end if;

        -- falling edge
        if sensor'event and sensor = '0' then
            if state = s_r_g then
                state <= s_g_r after 15 ns;
            end if;
        end if;
    end process;

    change_state:
    process (state)
    begin
        case state is
            when s_g_r => trafficlights <= "10001";
            when s_y_r => trafficlights <= "01001";
            when s_r_g => trafficlights <= "00110";
        end case;
    end process;

end Behavioral;
```

Testbench code:

```
library IEEE;
```

```

use IEEE.STD_LOGIC_1164.ALL;

entity my_system_tb is
end my_system_tb;


architecture Behavioral of my_system_tb is
    signal trafficlights : std_logic_vector(4 downto 0);
    signal sensor : std_logic;
begin
    mytlc: entity work.my_system port map (trafficlights => trafficlights, sensor => sensor);

    -- sensor <= '0', '1' after 5 ns, '0' after 20 ns, '1' after 23 ns, '0' after 27 ns;
    -- sensor <= '0', '1' after 5 ns, '0' after 8 ns, '1' after 23 ns, '0' after 27 ns;
    sensor <= '0', '1' after 5 ns, '0' after 8 ns, '1' after 9 ns, '0' after 27 ns;

end Behavioral;

```

Output:

 

پایان